

Assignment One (10%)

1. Discuss the following points briefly and you will present your work in the classroom.


A. Semiconductor materials and their types (**Group-1**)

B. Semiconductor diodes and their applications (**Group-2**)


C. Bipolar junction transistors (**Group-3**)

D. Field effect transistors (**Group-4**)

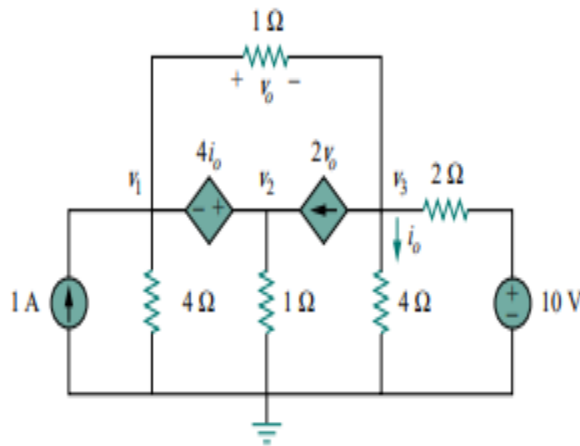2. Determine the node voltages for the circuit below. (You have to calculate using the necessary steps).



(a)

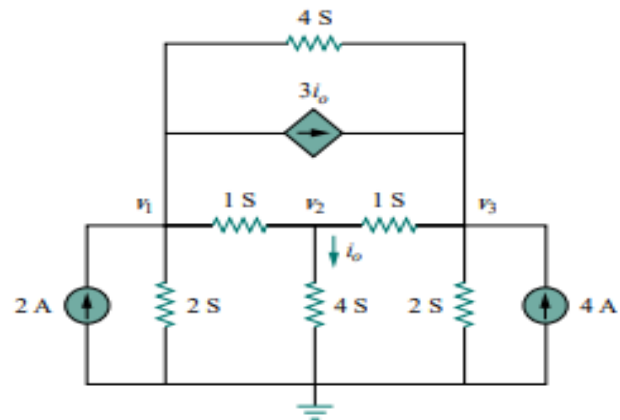

(b)